
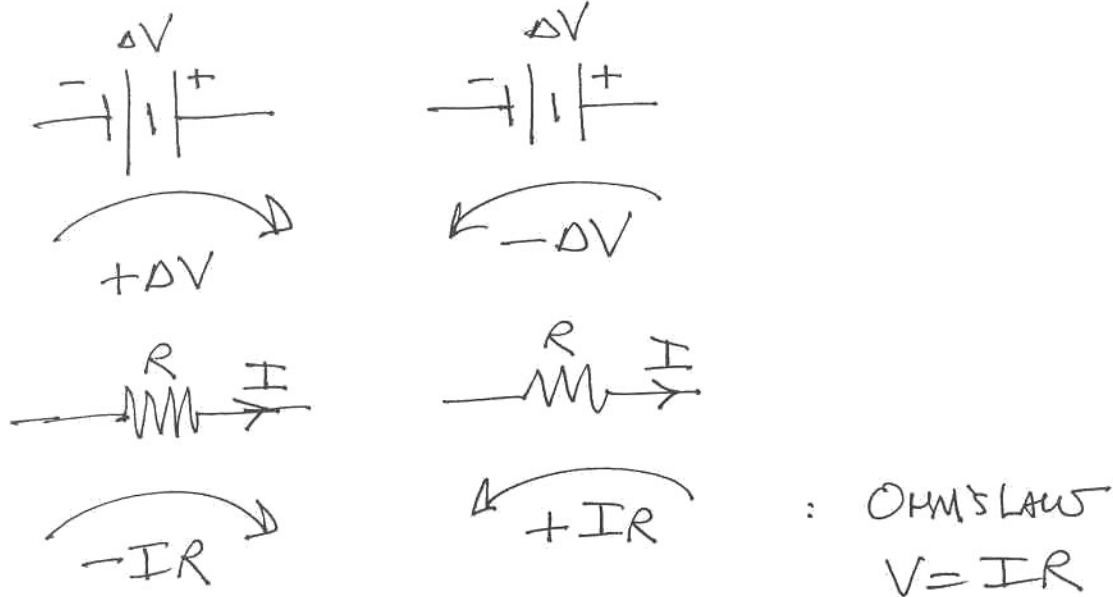


⑥ KIRCHHOFF LOOP VOLTAGES

(* CURVED ARROW SHOWS LOOP DIRECTION)

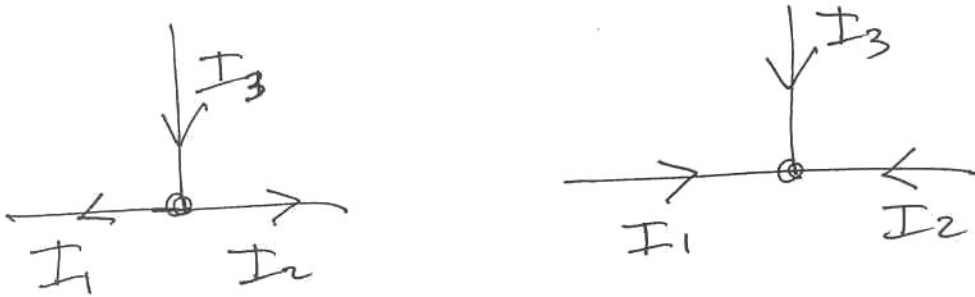

⑦ KIRCHHOFF JUNCTION CURRENTS




$$I_3 = I_1 + I_2$$

$$I_3 + I_1 + I_2 = 0$$

⑧ VOLTAGES AROUND A LOOP ADD UP TO ZERO

⑨ CURRENTS INTO A JUNCTION ADD UP TO ZERO

PRACTICE CIRCUIT (1)

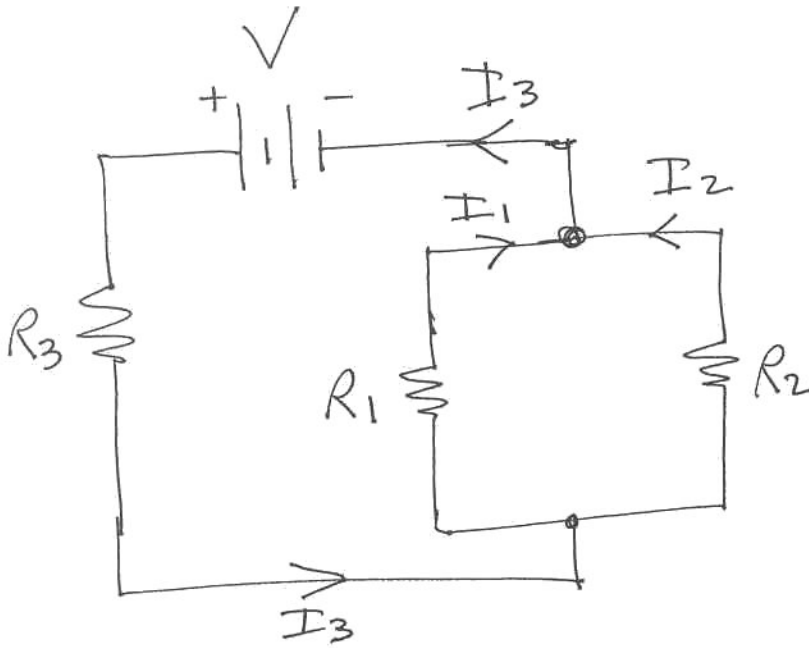

$$V = \underline{\hspace{2cm}}$$

$$R_1 = \underline{\hspace{2cm}}$$

$$R_2 = \underline{\hspace{2cm}}$$

$$R_3 = \underline{\hspace{2cm}}$$

⊙ THEORY : COMBINE RESISTANCE + OHM'S LAW

$$R_{12} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \underline{\hspace{2cm}}$$

$$R = R_{12} + R_3 = \underline{\hspace{2cm}}$$


$$I_3 = V/R = \underline{\hspace{2cm}}$$

$$\Delta V_3 = I_3 R_3 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \Delta V_2 = V - \Delta V_3 = \underline{\hspace{2cm}}$$

$$I_1 = \Delta V_1 / R_1 = \underline{\hspace{2cm}}$$
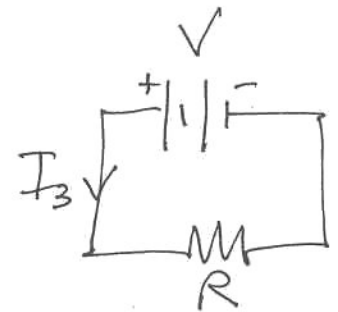
$$I_2 = \Delta V_2 / R_2 = \underline{\hspace{2cm}}$$



PRACTICE CIRCUIT (2)

© EXPERIMENT: MEASURE I_1, I_2, I_3 AND
 $V, \Delta V_1, \Delta V_2, \Delta V_3$

	THEORY	EXP	% DIFF
I_1			
I_2			
I_3			

	THEORY	EXP	% DIFF
V			
ΔV_1			
ΔV_2			
ΔV_3			

% DIFF (MAX) = _____


© CHECK KIRCHHOFF

LOOP 1 : $V - \Delta V_3 - \Delta V_1 =$ _____

LOOP 2 : $V - \Delta V_3 - \Delta V_2 =$ _____

JUNCTION : $I_3 - I_1 - I_2 =$ _____

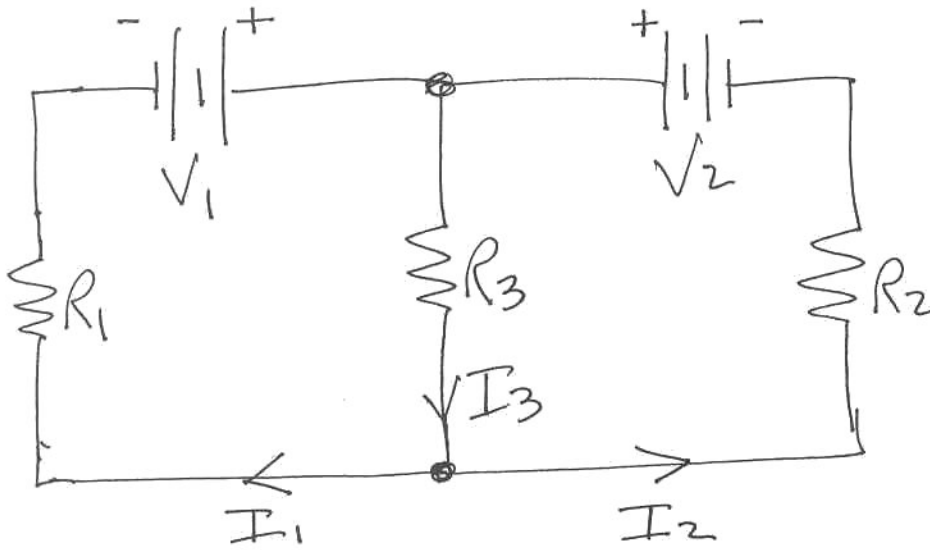KIRCHHOFF CIRCUIT (A) : BATTERIES ALIGNED
(THROUGH R_3)



$V_1 =$ _____

$V_2 =$ _____

$R_1 =$ _____

$R_2 =$ _____

$R_3 =$ _____

RESULTS (SHOW ALL CALCULATIONS)

$I_1(\text{THEO}) =$ _____ $I_1(\text{EXP}) =$ _____ % DIFF = _____


$I_2(\text{THEO}) =$ _____ $I_2(\text{EXP}) =$ _____ % DIFF = _____

$I_3(\text{THEO}) =$ _____ $I_3(\text{EXP}) =$ _____ % DIFF = _____

* MAXIMUM % DIFF = _____

* % UNC = _____

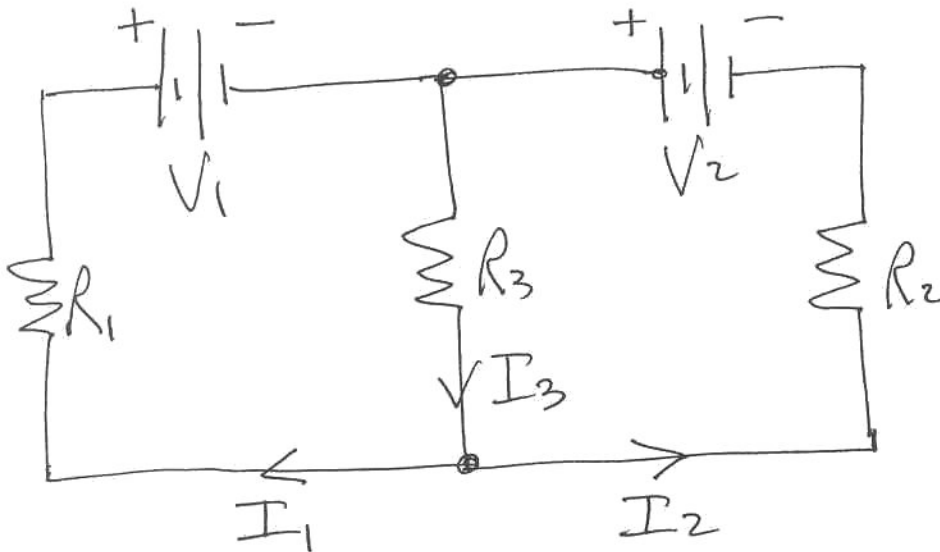KIRCHHOFF CIRCUIT (B): BATTERIES ANTI-ALIGNED
(THROUGH R_3)



$V_1 =$ _____

$R_1 =$ _____

$V_2 =$ _____

$R_2 =$ _____

$R_3 =$ _____

RESULTS (SHOW ALL CALCULATIONS)

I_1 (THEO) = _____ I_1 (EXP) = _____ % DIFF = _____

I_2 (THEO) = _____ I_2 (EXP) = _____ % DIFF = _____

I_3 (THEO) = _____ I_3 (EXP) = _____ % DIFF = _____

* MAXIMUM % DIFF = _____

* % UNC = _____